



Topic Test: OxfordAQA
International AS level Physics
Electricity

Name: _____

Class: _____

Date: _____

Time: **56 minutes**

Marks: **37 marks**

Comments:

1

During a lightning strike, 9.4×10^{18} electrons move from a cloud to the ground in a time of $18 \mu\text{s}$.

- (a) Calculate the current in the lightning strike due to the transfer of electrons.

current = _____ A

(2)

- (b) State the direction of the conventional current during this lightning strike.

(1)


(Total 3 marks)

2

- (a) Define resistance.

(1)

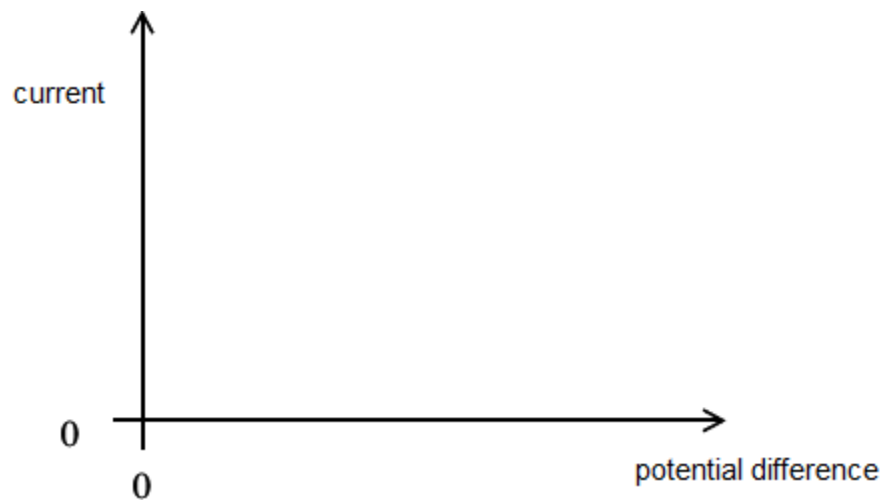- (b) (i) Sketch onto the axes below a graph of the variation of current with potential difference for a filament lamp.



(1)


- (ii) State and explain, in terms of electron flow, how the resistance of the filament lamp changes as the current in the lamp increases.

(3)

(Total 5 marks)

3

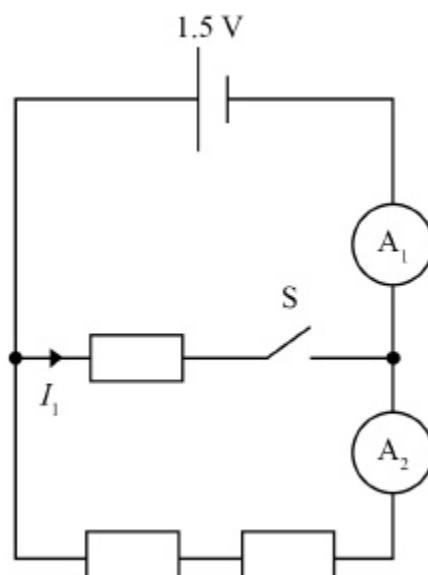The diagram shows three identical resistors, each with a resistance R , in a circuit connected to a cell with emf 1.5 V . The cell has negligible internal resistance.



- (a) When switch S is closed the reading of ammeter A_1 is 1.2 A and the reading of ammeter A_2 is 0.40 A

State the value of the current I_1 when switch S is closed.

$$I_1 = \underline{\hspace{2cm}} \text{ A}$$

(1)

- (b) Calculate R .

$$R = \underline{\hspace{2cm}} \Omega$$

(1)

- (c) Switch S is returned to the open position.

State and explain the effect this has on the readings of A_1 and A_2 .

(3)

(Total 5 marks)

Figure 1 shows a circuit used to determine the emf and internal resistance of a cell.

Figure 1


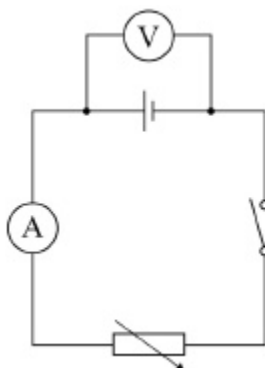


Figure 2 shows the variation of the voltmeter reading with current in the circuit as the variable resistor is adjusted.

Figure 2

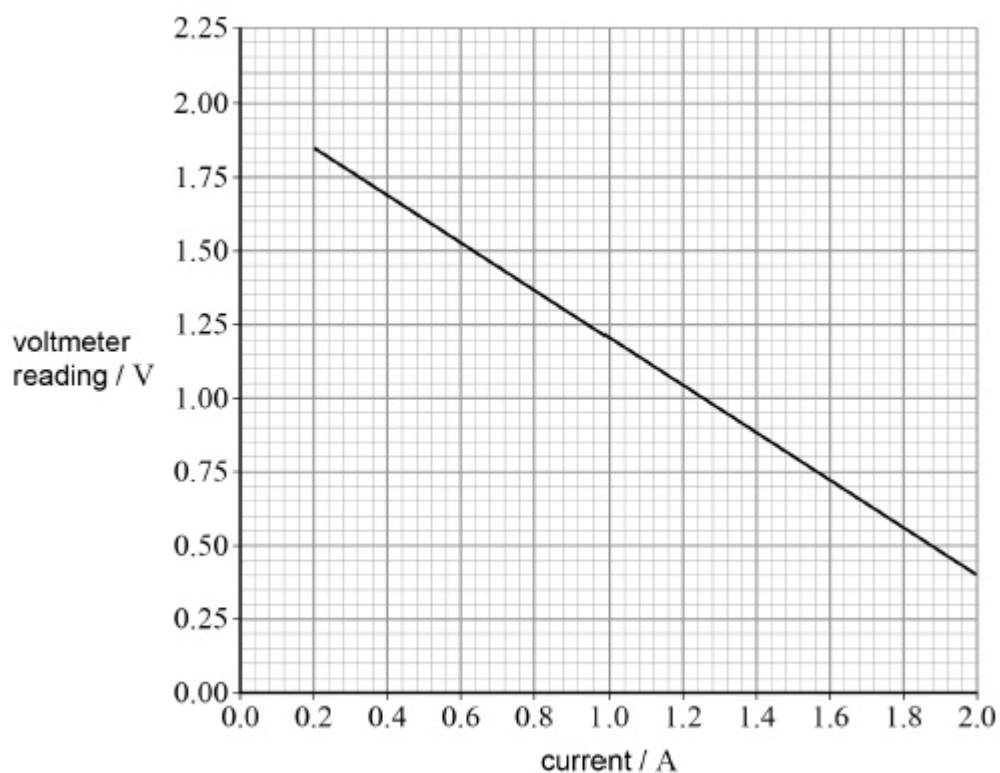

- (a) The circuit contains an ideal voltmeter and an ideal ammeter.

State the resistance of an ideal voltmeter.

(1)

- (b) Show that the internal resistance of the cell is approximately $0.8 \, \Omega$.

(1)

- (c) The variable resistor is adjusted until the current in the circuit is $2.10 \, \text{A}$.

Calculate the resistance of the variable resistor.

resistance = _____ Ω

(3)

(Total 5 marks)

5

A fuse wire is a short piece of wire in series with a component in a circuit. The fuse wire is designed to melt and act as a circuit breaker when the current exceeds a safe level. A lighting technician needs to choose a fuse wire for a spotlight that normally operates at $11 \, \text{A}$. He can choose from two types of fuse wire, **A** and **B**, shown in the table below. Each fuse wire is $1.2 \, \text{cm}$ long.

Fuse wire	Metal	Resistivity /	Cross-sectional area / m^2	Power required to melt fuse wire / W
A	Zinc	5.5×10^{-8}	1.8×10^{-8}	2.4
B	Silver	1.6×10^{-8}	9.5×10^{-9}	2.7

- (a) Complete the table above with the SI unit of resistivity.

(1)

- (b) Determine which fuse wire should be used for the spotlight.

fuse wire = _____

(4)

- (c) Suggest **one** other factor that might influence the technician's choice.

(1)


(Total 6 marks)

6

Figure 1 shows a thermistor **T** used in an alarm circuit for a refrigerator. The alarm is designed to sound a buzzer **B** when the temperature exceeds a threshold value. **B** has a constant resistance of $123\ \Omega$.

The battery has a negligible internal resistance.

Figure 1

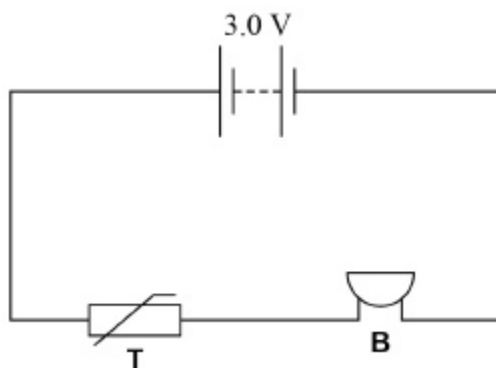

The buzzer sounds when the potential difference across it is greater than 1.8 V.

- (a) Explain why the potential difference across the buzzer increases when the temperature increases.


(3)

- (b) Show that, when the potential difference across the buzzer is 1.8 V, the resistance of the thermistor is about $80\ \Omega$.

(2)

Figure 2 shows how the resistance of the thermistor varies with temperature over a small range of temperatures.

Figure 2

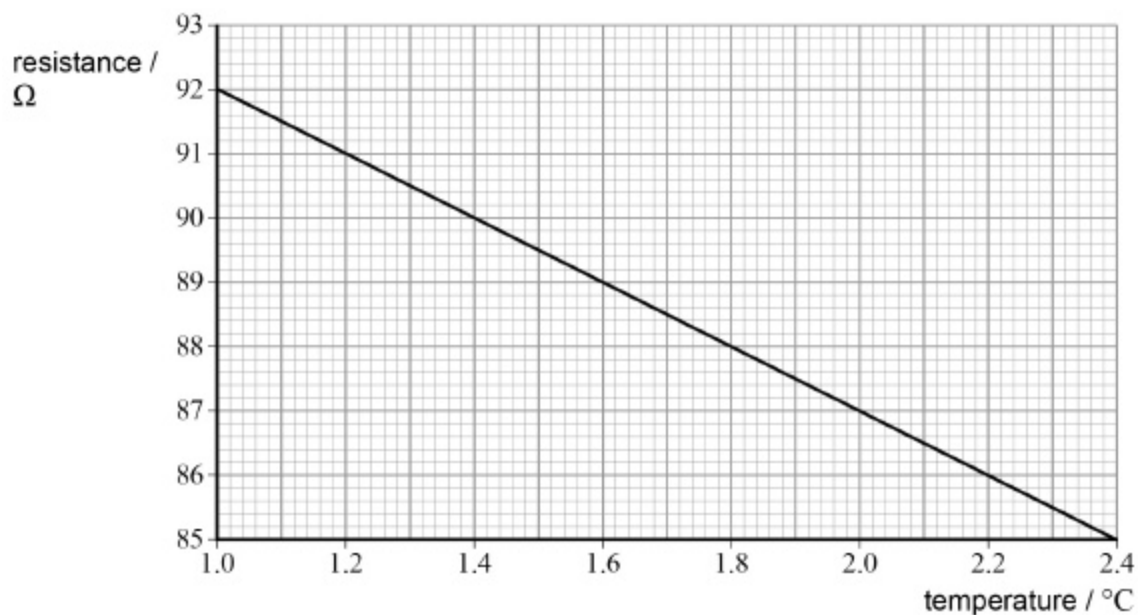

(c) Calculate the gradient of the graph.

gradient = _____ $\Omega \text{ K}^{-1}$

(2)

- (d) Determine the temperature at which the buzzer will start to sound.
Assume that the gradient of the graph remains constant when the temperature rises above $2.4\text{ }^{\circ}\text{C}$.

temperature = _____ $^{\circ}\text{C}$

(1)

(Total 8 marks)

7

What is a unit for potential difference?

A $\text{A } \Omega^{-1}$

☐

B C J^{-1}

☐

C $\text{J A}^{-1} \text{s}^{-1}$

☐





D W A

☐

(Total 1 mark)

8


Which network of resistors has the largest total resistance?

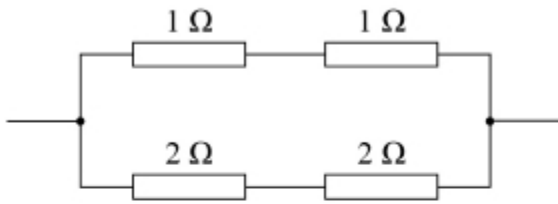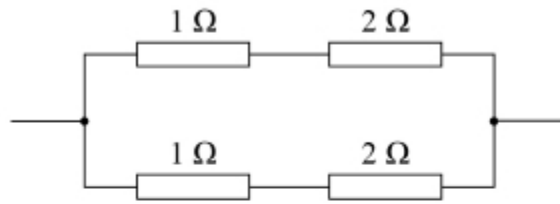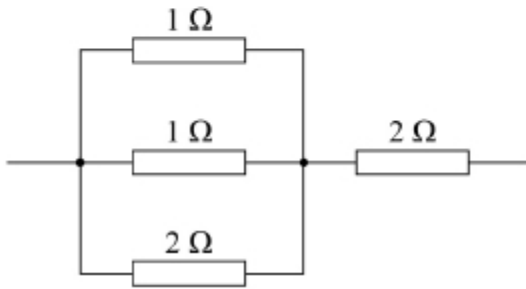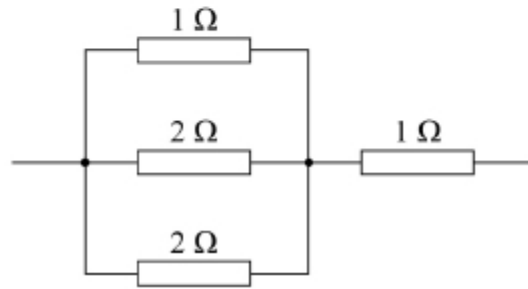A**B****C****D****A** ☐**B** ☐**C** ☐**D** ☐

(Total 1 mark)

9

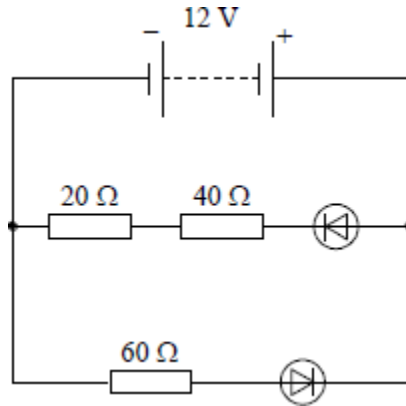The 12 V battery in the circuit shown has negligible internal resistance. The diodes have 'ideal' characteristics.




The current through the battery is approximately

- A 0 A
- B 0.10 A
- C 0.20 A
- D 0.40 A

(Total 1 mark)

10

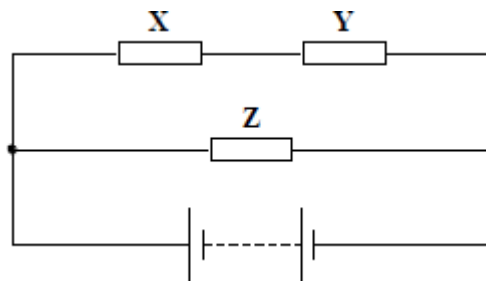Three identical resistors **X**, **Y** and **Z** are connected across a battery as shown.




The ratio $\frac{\text{power developed in X}}{\text{power developed in Z}}$ is

- A $\frac{1}{4}$
- B $\frac{1}{2}$
- C 1
- D 2

(Total 1 mark)

11

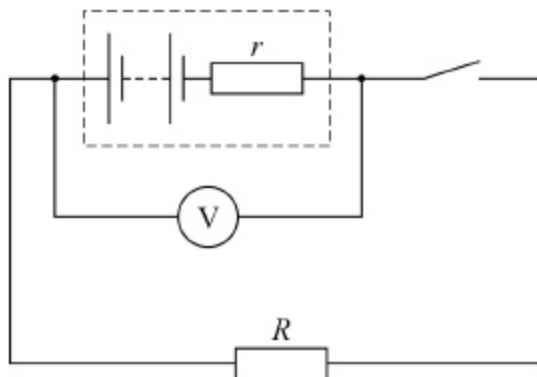The diagram shows a 12 V battery connected to a resistor of resistance R . The voltmeter reads 10 V when the switch is closed.



What is the internal resistance r of the battery?

A $\frac{R}{6}$ ☐

B $\frac{R}{5}$ ☐

C $5R$ ☐

D $6R$ ☐

(Total 1 marks)

Mark schemes

1	(a) $I = Q/t = 9.4 \times 10^{18} \times 1.6 \times 10^{-19} / 18 \times 10^{-6} \checkmark$ $= 84\,000\text{ A (83\,556 A)} \checkmark$	2	1	[3]
	(b) Up/upwards/from ground to cloud $\checkmark$			
2	(a) ratio of voltage (across component) to current (through component) or $R = V/I$ with terms defined and R as subject	B1	1	[5]
	(b) (i) correct curve	B1	1	
	(ii) resistance increases / increase in resistivity	B1		
	energy transfer increases lattice vibration / temperature rise increases lattice vibration / electron collisions increases lattice vibration	B1		
	more frequent collisions/ ions now a larger target for electrons	B1	3	
3	(a) $I_1 = 0.80\text{ A}$ <i>Accept 1 sig. fig. in this case</i>		1	
	(b) $R = 1.9\ \Omega$		1	

(c) effect : Reading of A_1 decreases

1

reason: because the total circuit resistance has increased
(reason marks are dependent on effect marks)

1

effect: Reading of A_2 remains constant

1

reason: The p.d. and resistance for this branch are constant.

Accept lower part of circuit is unaffected by the switch

1

Max 3

Alternative:

$$A_1 = A_2$$

1

Total circuit resistance = $2R$

1

Current = 0.40 A

1

So A_1 decreases (A_2 stays the same)

1

Max 3

[6]

4

(a) infinite ✓

Condone "very large"

1

(b) Evidence of using graph to get gradient

OR

use of intercept (2 V) and a data point e.g (1, 1.2) ✓

Must be a correct pair of coordinates.

1

(c) $E = 2.00 \text{ (V)}$ ✓

Substitution into $E = I(R + r)$ (e.g candidate's $E = 2.1(R + 0.8)$) ✓

$0.15(2) \text{ (}\Omega\text{)}$ ✓

OR

Total $R = 2.00/2.1 = 0.95$ ✓

$R = 0.95 - 0.8$ ✓

$0.15(2) \text{ (}\Omega\text{)}$ ✓

Alternative method:

*Deduce pd correctly (0.32 V) and substitute into $R = V/I$
 $= 0.32/2.1$*

Allow reasonable range for data extraction

Allow 1 max for any extrapolation done by extending the grid and line but reward a "mathematical" extrapolation such as using similar triangles.

3

[5]

5

(a) Ωm

1

(b) Use of $R = \rho l/A$ seen

Allow reverse argument i.e. calculating power needed to melt fuses starting from 11 A

Correct value for at least 1 resistance (zinc 0.037Ω , silver 0.020Ω) ✓

Use of $P = I^2R$ with a correct substitution of their R ✓

Correct value for both currents (8.1 A for zinc 11.6 A for silver) or powers and statement justifying the use of silver ✓

4

(c) Any sensible factor eg corrosion, cost, availability

1

[6]

6

(a) As temperature increases, the resistance of the thermistor decreases ✓

As more charge carriers become available for conduction/ are raised to the conduction band ✓

A larger share/proportion of the battery pd across the buzzer (or reference to a potential divider) ✓

3

- (b) Use of $\frac{1.2}{1.8} = \frac{R}{123}$ or $I = \frac{1.8}{123}$ or $I = 0.0146$ (A) ✓

Must see 82 not just 80. Answers based on checking can only score both marks if unrounded values are seen.

$$R = 82 (\Omega) \checkmark$$

2

- (c) Attempt to find gradient as $\Delta y / \Delta x$ with correct values read from graph

$$\text{Gradient} = -5 (\Omega \text{ K}^{-1})$$

Must have negative sign for second mark.

2

- (d) $T = 3.0$ (°C)

1

[8]

7 C

[1]

8 C

[1]

9 C

[1]

10 A

[1]

11 B

[1]